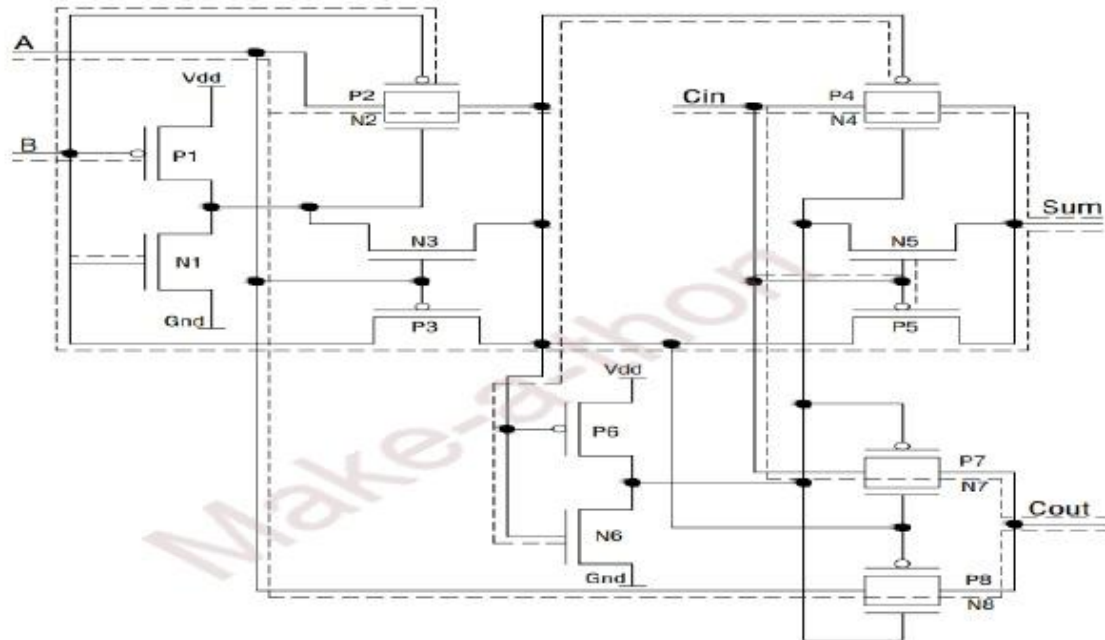



## Adder 6

Circuit to be implemented



Implementation in cadence

Before sizing

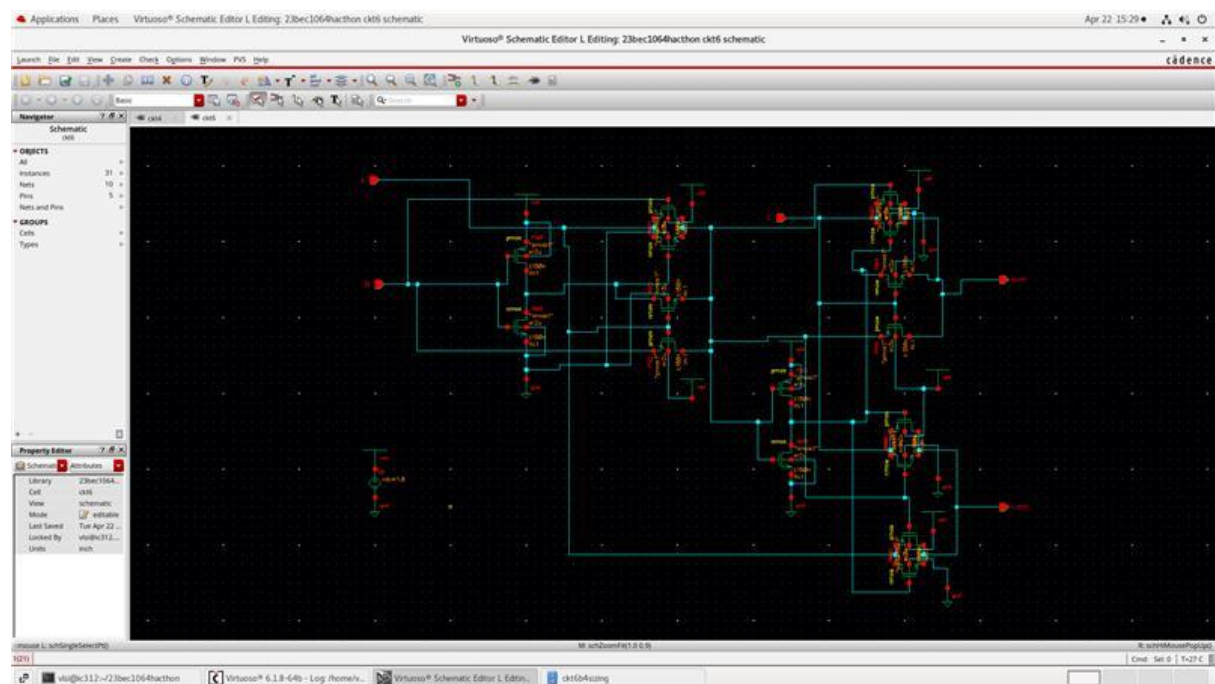

## Timing diagram




## Power



## Delay value


## Sum

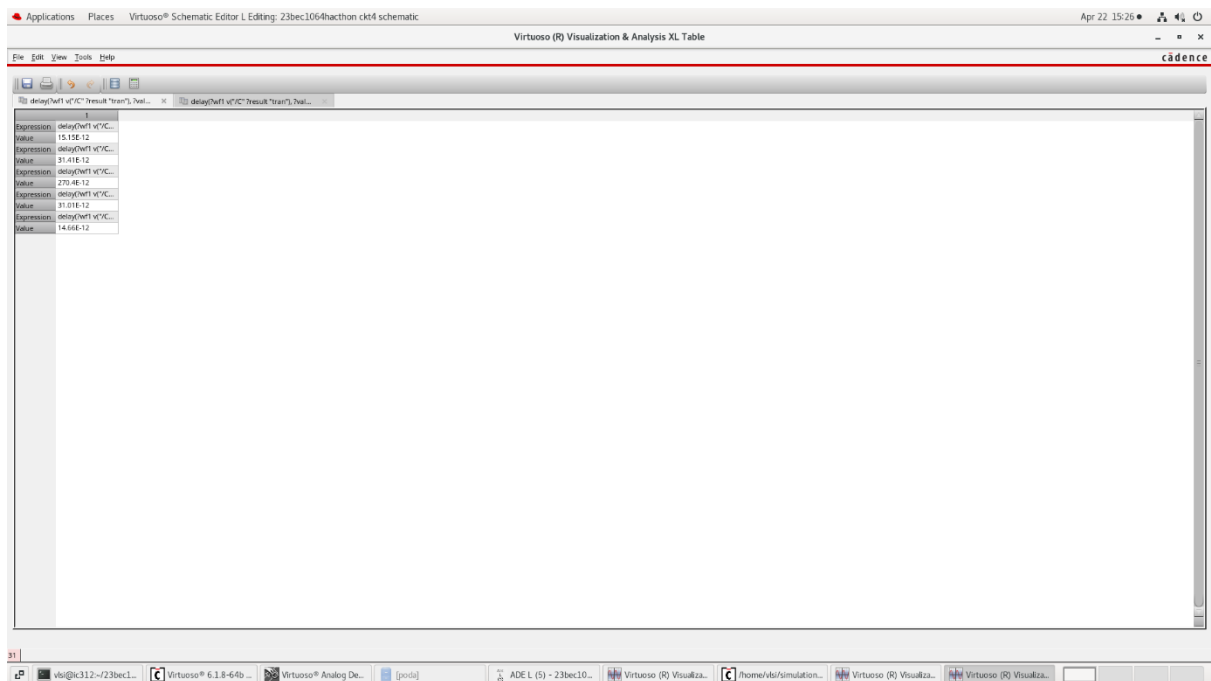

The screenshot shows the Virtuoso (R) Visualization & Analysis XL Table window. The table displays simulation results for delay values. The first column is labeled 'Expression' and the second is 'Value'.

Expression	Value
delay[0w1 v1]C...	15.15E-12
delay[0w1 v1]C...	31.41E-12
delay[0w1 v1]C...	270.4E-12
delay[0w1 v1]C...	31.01E-12
delay[0w1 v1]C...	14.64E-12


## Carry

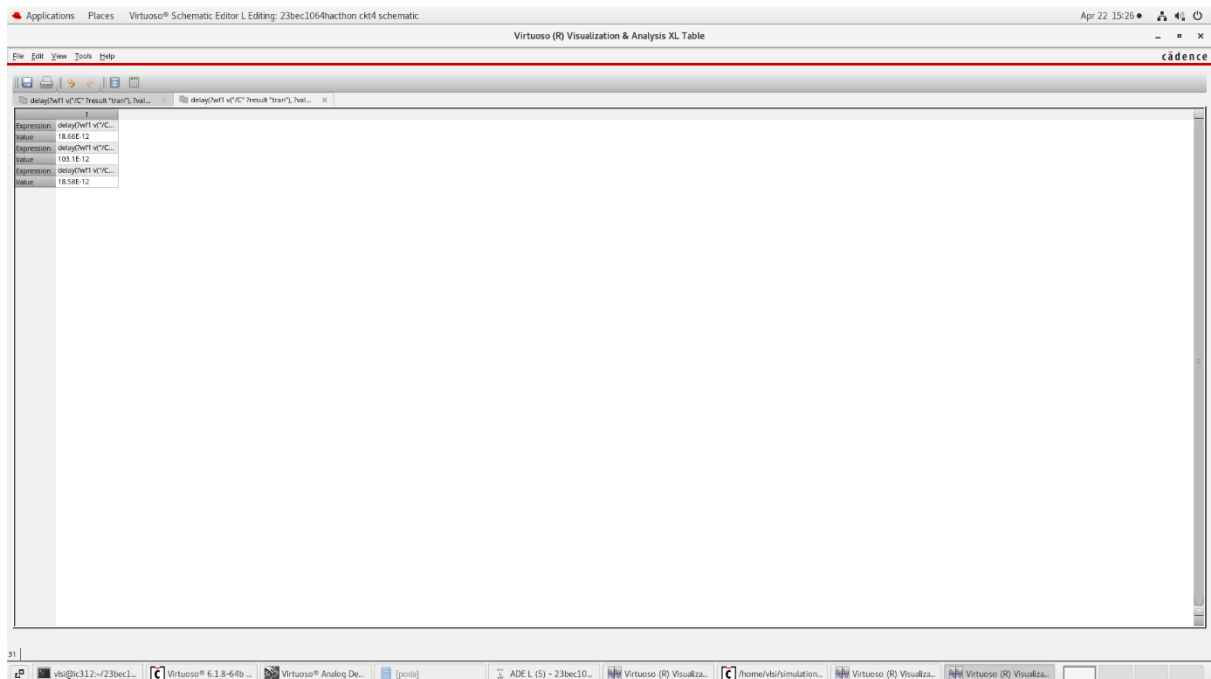


The screenshot shows the Virtuoso (R) Visualization & Analysis XL Table window. The table displays simulation results for carry values. The first column is labeled 'Expression' and the second is 'Value'.

Expression	Value
delay[0w1 v1]C...	18.66E-12
delay[0w1 v1]C...	105.1E-12
delay[0w1 v1]C...	18.58E-12

## Power calculation

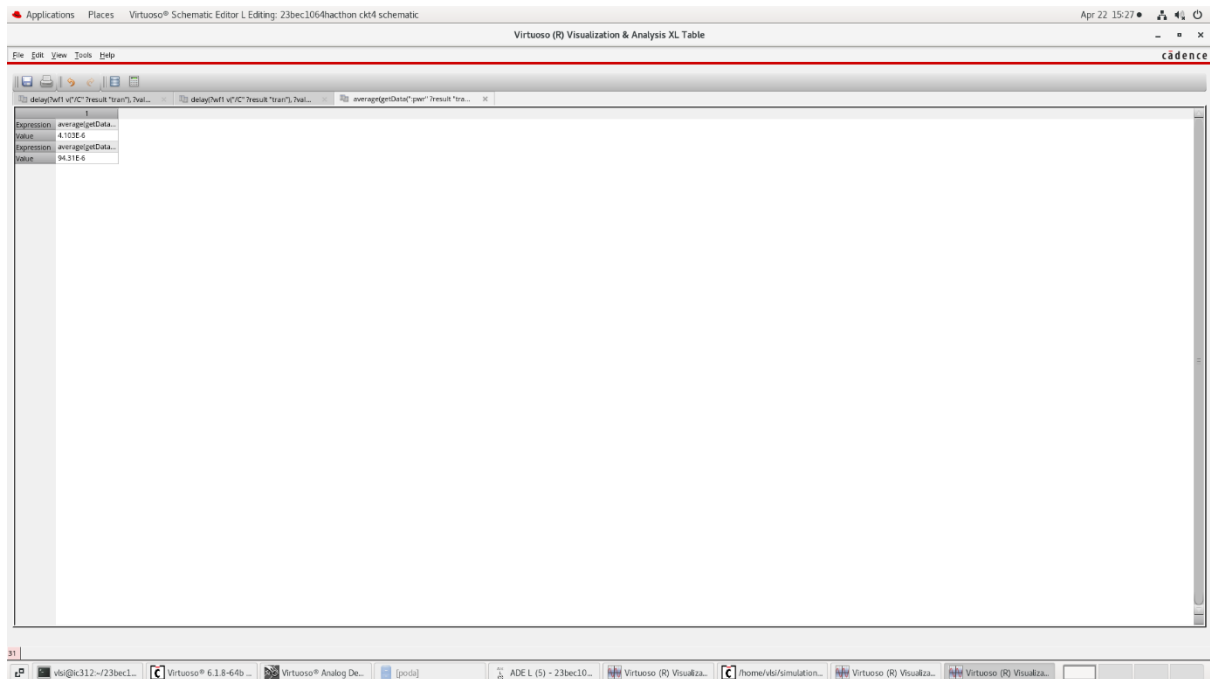


## after sizing

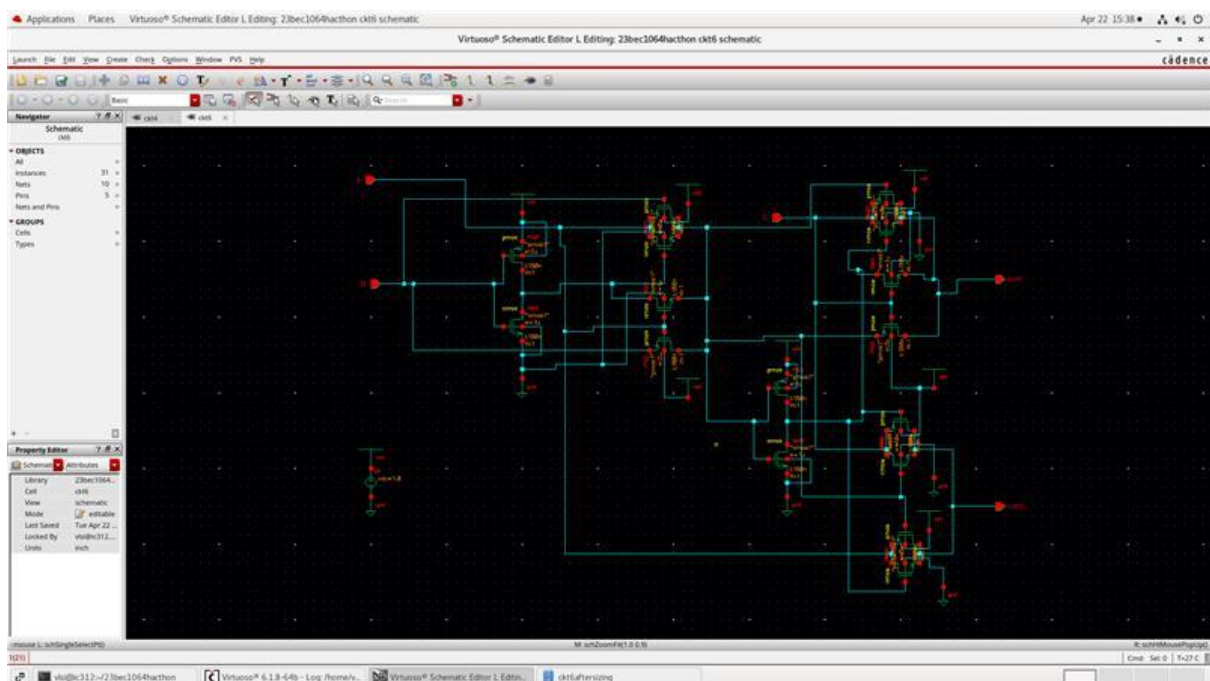



## Timing diagram

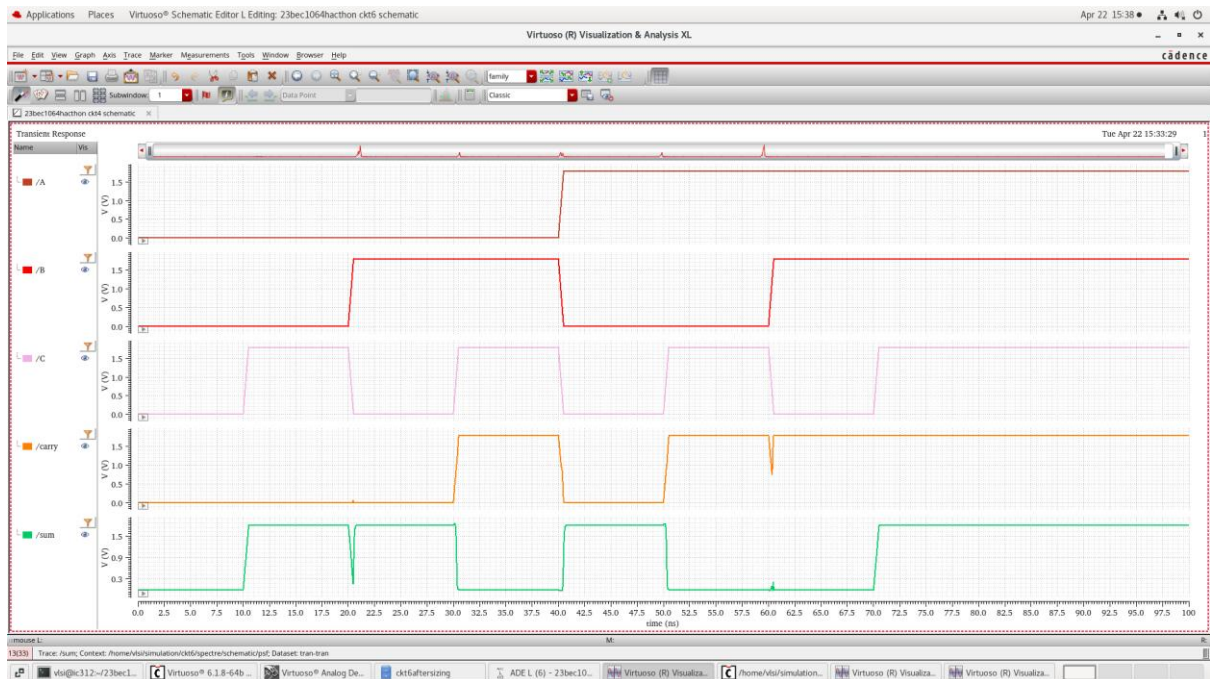


## Power



## Delay value


## Sum

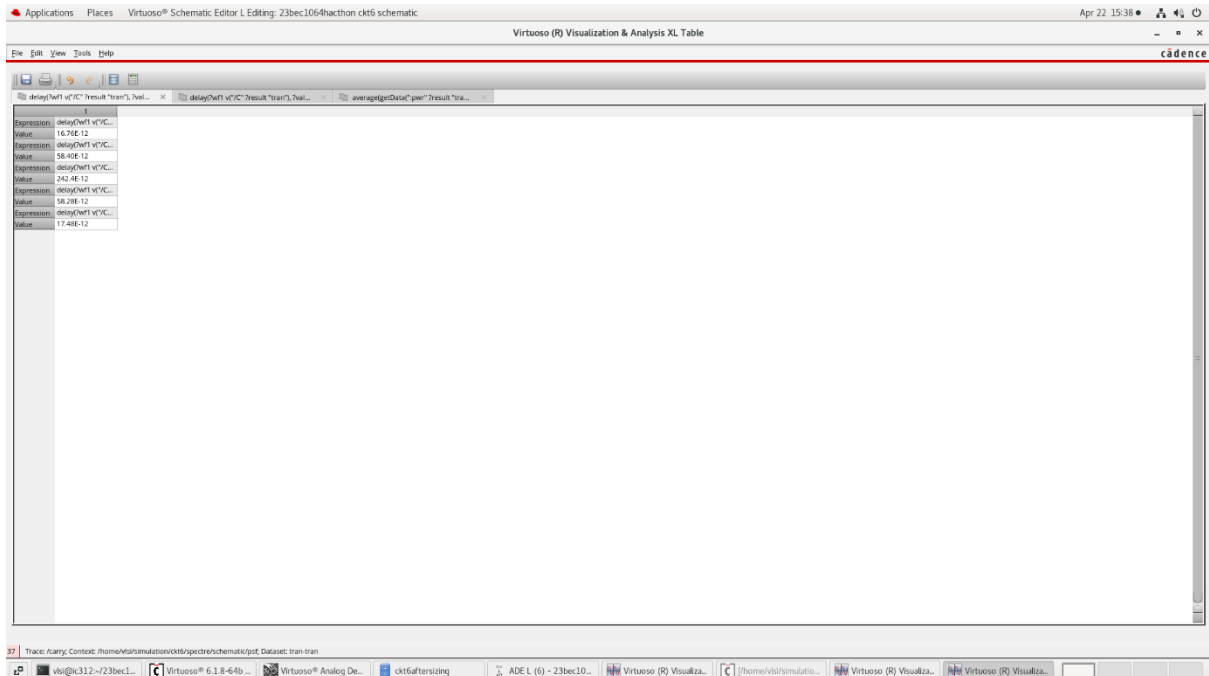

The screenshot shows the Cadence Virtuoso (R) Visualization & Analysis XL Table. The table displays the following data:

Expression	Value
delay(tw1 v1)C...	16.74E-12
delay(tw1 v1)C...	58.40E-12
delay(tw1 v1)C...	242.4E-12
delay(tw1 v1)C...	58.28E-12
delay(tw1 v1)C...	17.40E-12


## Carry

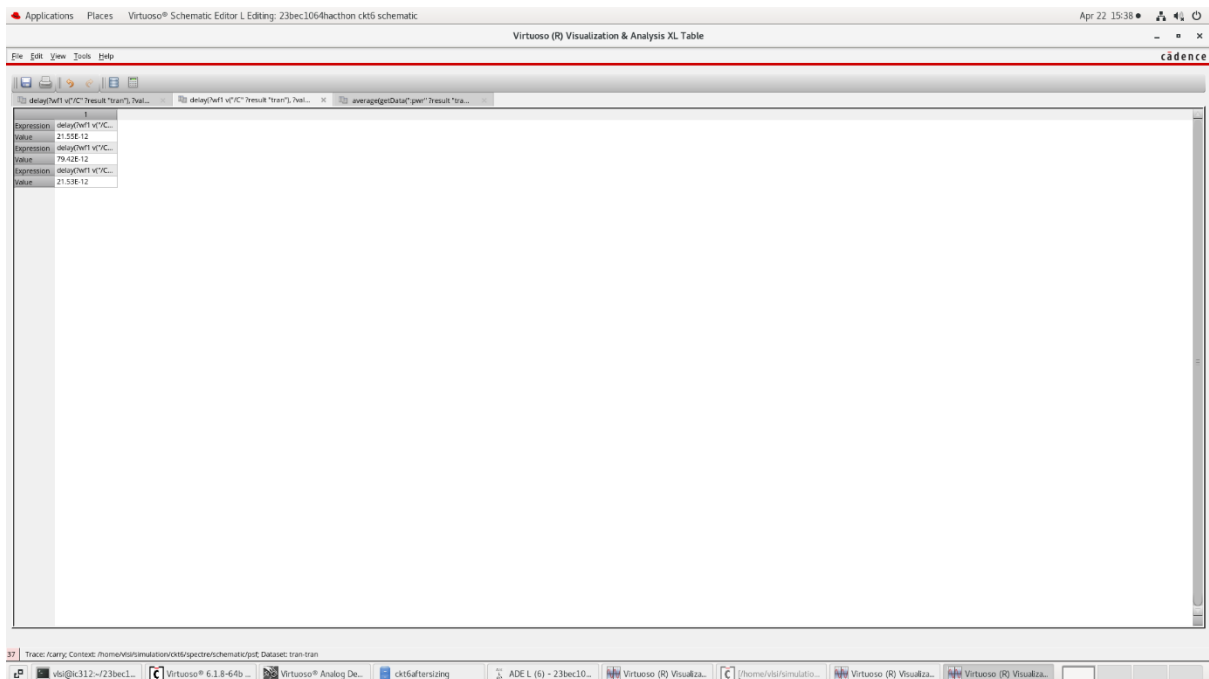

The screenshot shows the Cadence Virtuoso (R) Visualization & Analysis XL Table. The table displays the following data:

Expression	Value
delay(tw1 v1)C...	21.55E-12
delay(tw1 v1)C...	79.42E-12
delay(tw1 v1)C...	21.53E-12

## Power calculation

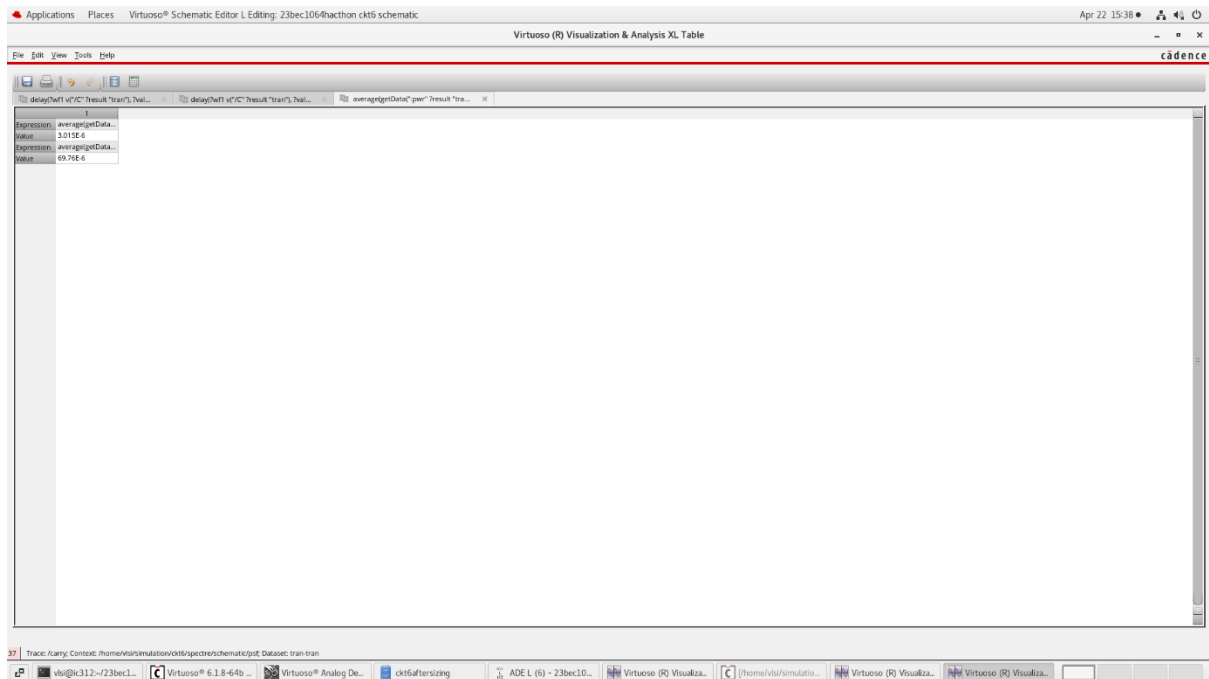

Folder 6:

Sum	Bit pattern	Delay (Before Sizing) (In seconds)	Delay (After Sizing) (In seconds)
	001B	15.15 E-12	16.76 E-12
	011B	31.41 E-12	58.4E-12
	100B	270.4 E-12	242.4E-12
	101B	31.01 E-12	58.28 E-12
	111B	14.66 E-12	17.48 E-12

Copy

Bit pattern	Delay (Before Sizing) (In seconds)	Delay (After Sizing) (In seconds)
011B	18.66 E-12	21.85 E-12
100B	103.1 E-12	79.42 E-12
101B	18.58 E-12	21.53 E-12

Power (Before Sizing) =  $4.103 \text{ E-6 W}$

Power (After Sizing) =  $3.015 \text{ E-6 W}$